$$R_{B} = 1M\Omega$$

$$R_{C} = 10V$$

$$R_{C} = 2k\Omega$$

$$I_{C}$$

$$I_{B}$$

$$\beta = 100$$

$$I_{E}$$

$$R_{E}$$

$$1k\Omega$$

$$I_{C}$$