				<b>—</b>	_
Clock	$Q_3$	$Q_2$	$Q_1$	$Q_0$	
	0	0	0	0	
1	0	0	0	1	1
2	0	0	1	1	3
3	0	1	1	1	7
4	1	1	1	1	15
5	1	1	1	0	14
6	1	1	0	0	12
7	1	0	0	0	8
8	0	0	0	0	0