$$V_{Th}$$
 $20V$ 
 $100\Omega$ 
 $100\Omega$ 
 $V_{Th} = \frac{150}{250} \times 20 = 12V$ 
 $R_{Th}$ 
 $S. c.$ 
 $100\Omega$ 
 $R_{Th} = \frac{100 \times 150}{250} = 60\Omega$